

APPLICATION NOTE

Matching Differential Port Devices

Introduction

Differential signaling is the primary choice for a low power RF interconnection because it provides superior immunity to noise by offering twice the signal swing for a given supply voltage. The out of phase property of a balanced pair has several other benefits: it rejects any common mode interference signal, cancels the even order distortions such as IM2, and reduces Electromagnetic Interference (EMI), EMI emission, and susceptibility.

However, this presents a challenge for RF designers to integrate differential devices together since the widely used S-parameter matching technique cannot simply be applied. Transmission line design is also different than a single-ended structure because of the differential mode of propagation.

This Application Note depicts a simple generic technique to match differential impedance devices and gives some matching circuit examples for the system shown in Figure 1 that uses the SKY65336-11 and SKY65337-11 Front-End Modules (FEMs). The results of differential matching are compared using elaborate tools such as a four-port network analyzer and ADS Electronics Design Automation (EDA) application software.

Refer to the respective Data Sheets for further information: SKY65336-11 (document #200939) and SKY65337-11 (document #200940).

Impedance Matching

Impedance matching is the practice of tuning a load impedance (Z) to the optimum impedance (Z_{OPT}) of a connected device (see Figure 2). This requires three main steps:

1. Find the optimum impedance, Z_{OPT} . This process is not detailed here but is usually achieved by tuning the load impedance of the circuit until the performance (i.e., the output power for a transmitter or the Noise Figure [NF] for a receiver) is met.
2. Measure the load impedance (Z) that needs to be matched (note that this is done in the same way that the optimum impedance is measured).
3. Determine the matching circuit that tunes the load (Z) to the optimum impedance, Z_{OPT} .


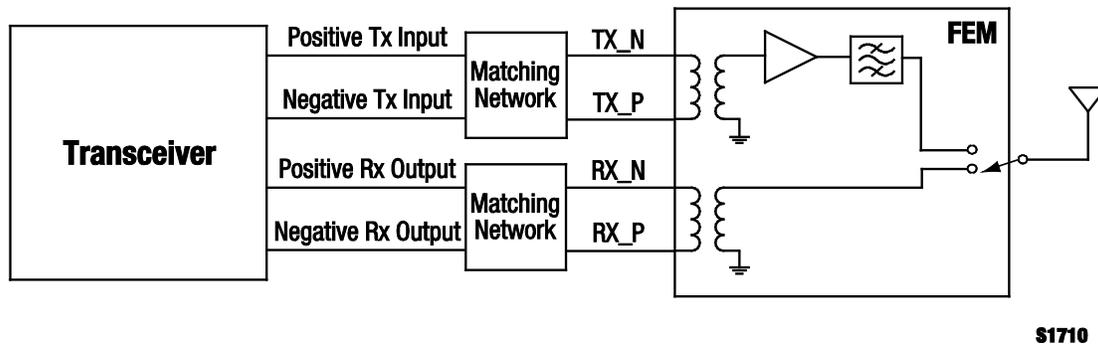


Figure 1. Example of a Differential Interconnection Between a Zigbee®- Compliant Transceiver and an FEM

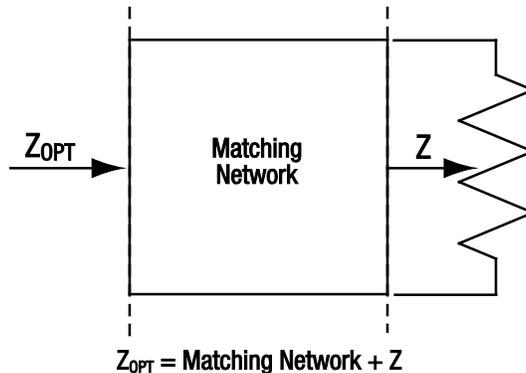

S1711

Figure 2. Impedance Matching

Differential Impedance Measurement

Basic Two-Port Circuit

A network analyzer is used to measure RF impedance. Each port of the two-port circuit shown in Figure 3 is alternately connected to a Z_o impedance source and a Z_o impedance load. The equipment measures and reports the matrix S_{sm} as shown in Equation 1, which represents the single mode (sm) scattering parameters. The variables a_1 and a_2 represent the incident waves, and b_1 and b_2 represent the reflected waves.

$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = S_{sm} \times \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} \quad (1)$$

Where:

$$S_{sm} = \begin{pmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{pmatrix}$$

The relationship between the S-parameters and the impedance is given by Equation 2:

$$Z_i = Z_o \times \frac{(1 + s_{ii})}{(1 - s_{ii})} \quad (i \in [1,2]) \quad (2)$$

Voltages and currents at the two nodes are calculated using Equation 3:

$$\begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} v_1^+ + v_1^- \\ v_2^+ + v_2^- \end{pmatrix} = \begin{pmatrix} Z_1 \times i_1 \\ Z_2 \times i_2 \end{pmatrix} = \begin{pmatrix} Z_1 \times (i_1^+ - i_1^-) \\ Z_2 \times (i_2^+ - i_2^-) \end{pmatrix} \quad (3)$$

Where v_i^+ and i_i^+ represent the forward voltage and current, respectively, and v_i^- and i_i^- represent the reverse voltage and current, respectively.

Extension to Differential Circuits: Different Modes of Transmission

For differential circuits, S-parameter theory has been extended to introduce the concept of mixed modes [Bockelman et. al. 1, 2]. Therefore, Figure 3 could represent either a two-port single ended circuit or a single-port mixed mode circuit.

The model has two modes of propagation: common mode and differential mode. For both modes, incident waves a_c , a_d , and reflected waves b_c , b_d , as well as voltages and currents v_c , v_d , i_c , and i_d are defined using Equations 4 through 10.

$$a_c = \frac{1}{\sqrt{2}}(a_1 + a_2) \text{ and } b_c = \frac{1}{\sqrt{2}}(b_1 + b_2) \quad (4)$$

$$a_d = \frac{1}{\sqrt{2}}(a_1 - a_2) \text{ and } b_d = \frac{1}{\sqrt{2}}(b_1 - b_2) \quad (5)$$


If:
$$M = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & -1 \\ 1 & 1 \end{pmatrix} \quad (6)$$

Then:
$$\begin{pmatrix} b_d \\ b_c \end{pmatrix} = M \times \begin{pmatrix} b_1 \\ b_2 \end{pmatrix} \text{ and } \begin{pmatrix} a_d \\ a_c \end{pmatrix} = M \times \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} \quad (7)$$

$$v_c = \frac{1}{2}(v_1 + v_2) \text{ and } i_c = (i_1 + i_2) \quad (8)$$

$$v_d = (v_1 - v_2) \text{ and } i_d = \frac{1}{2}(i_1 - i_2) \quad (9)$$

$$\begin{pmatrix} v_d \\ v_c \end{pmatrix} = \begin{pmatrix} Z_d \times i_d \\ Z_c \times i_c \end{pmatrix} \quad (10)$$

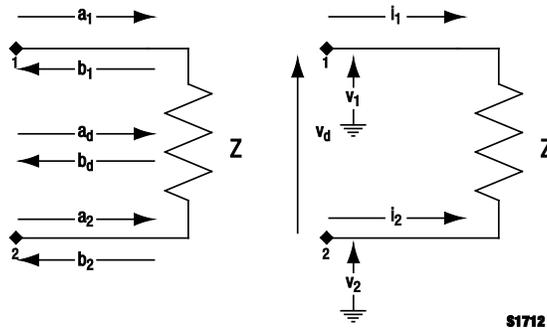
Figure 3. Single and Differential Mode Power Wave and Voltage/Current Circuit Representations

Mixed mode S-parameters are defined by:

$$\begin{pmatrix} b_d \\ b_c \end{pmatrix} = S_{mm} \times \begin{pmatrix} a_d \\ a_c \end{pmatrix} \quad (11)$$

Where S_{mm} is defined by:

$$S_{mm} = \begin{pmatrix} s_{dd} & s_{cd} \\ s_{dc} & s_{cc} \end{pmatrix} \quad (12)$$

And: S_{dd} = differential mode S-parameter, needed to determine the differential impedance.

S_{cc} = common mode parameter.

S_{dc} , S_{cd} = cross mode parameters.

Each of the cross mode parameters represent the amount of transfer from common to differential mode, and vice versa, that propagates through the circuit. For an ideal balanced circuit, note that the mixed terms S_{dc} and S_{cd} are zero.

The goal is to determine the differential mode circuit impedance Z_d . For this purpose, only the differential mode propagation needs be evaluated (common mode propagation can be omitted). There is no RF common source ($a_c = 0$) even if the DC supply can be present on each side of the balanced port.

Bockelman et. al. [2] demonstrate that mixed mode parameters can be derived from single mode parameters:

$$(S_{mm}) = M \times S_{sm} \times M^{-1} \quad (13)$$

Therefore, S_{mm} can be redefined as:

$$(S_{mm}) = \frac{1}{2} \times \begin{pmatrix} s_{11} - s_{12} - s_{21} + s_{22} & s_{11} + s_{12} - s_{21} - s_{22} \\ s_{11} - s_{12} + s_{21} - s_{22} & s_{11} + s_{12} + s_{21} + s_{22} \end{pmatrix} \quad (14)$$

Assuming the circuit shown in Figure 3 is perfectly balanced, S_{11} and S_{22} are equal as are S_{12} and S_{21} . Therefore, from Equation 14, S_{dc} and S_{cd} are zero. Since S-parameters always normalize to a reference impedance, it is necessary to determine the value of the differential reference impedance Z_{0d} . It is intuitively easy to determine. For a single mode operation, the reference (or characteristic) impedance is defined by:

$$Z_0 = \frac{v_i^+}{i_i^+} = -\frac{v_i^-}{i_i^-} \quad (15)$$

Similarly, for a differential case:

$$Z_{0d} = \frac{v_d^+}{i_d^+} = -\frac{v_d^-}{i_d^-} \quad (16)$$

Or:

$$Z_{0d} = \frac{v_1^+ - v_2^+}{\frac{1}{2}(i_1^+ - i_2^+)}$$

If the circuit is matched, there is no return current. Therefore, according to Kirchoff's Law:

$$i_1^+ = -i_2^+$$

Therefore:

$$Z_{0d} = \frac{v_1^+ - v_2^+}{i_1^+} = \frac{v_1^+}{i_1^+} + \frac{v_2^+}{-i_1^+} = \frac{v_1^+}{i_1^+} + \frac{v_2^+}{i_2^+}$$

Or:

$$Z_{0d} = 2 \times Z_0 \quad (17)$$

Using Equation 2, differential impedance can be expressed as:

$$Z_d = Z_{0d} \times \frac{(1 + s_{dd})}{(1 - s_{dd})} \quad (18)$$

From Equations 14 and 17, Z_d can be defined as:

$$Z_d = 2Z_0 \times \frac{(2 + s_{11} - s_{12} - s_{21} + s_{22})}{(2 - s_{11} + s_{12} + s_{21} - s_{22})} \quad (19)$$

Using the SKY65336-11 FEM, the normalized (50 Ω reference impedance) 2450 MHz single mode S-parameters of the differential transmit input were measured using a network analyzer and plugged into Equation 1:

$$S_{sm} = \begin{pmatrix} 0.083 + j \times 0.478 & 0.372 + j \times 0.199 \\ 0.361 + j \times 0.207 & -0.0714 + j \times 0.675 \end{pmatrix}$$

APPLICATION NOTE • MATCHING DIFFERENTIAL PORT DEVICES

Solving Equation 12 for S_{dd} where the differential reference impedance, Z_{0d} , is 100Ω :

$$S_{dd} = -0.361 + j \times 0.374$$

And solving Equation 19 for Z_d :

$$Z_d = 36.6 + j \times 37.5 \Omega$$

The differential mode S-parameter, S_{dd} , was also simulated using the ADS EDA application software. The results were plotted on a Smith Chart as shown in Figure 4. The single-mode, S-parameters derived with software simulation agreed with measurements using a four-port network analyzer.

Matching With Differential Impedance

The process of matching involves tuning the impedance (determined as described in the previous section) to a given impedance.

The use of discrete inductors and capacitors is an easy way to achieve impedance matching. If area is not a constraint, using transmission lines and stub tuner elements is a cost-competitive

alternate solution. This method provides a lower loss but is not as flexible as using discrete elements since new matching means a new PCB design.

In both cases, the Smith Chart is a powerful and simple graphical tool that allows the navigation from one impedance to another, adding series and parallel matching elements.

Using a shunt element, a balanced circuit keeps its symmetry because the element is placed between the two ports. When a series component is introduced, the circuit is no longer symmetrical.

As shown in Figure 5, when the lumped elements Land C are added to the balanced load, Z (S11 and S22 are equal), S1'1' and S2'2' of the matched load, Z_{opt} , are now different.

Based on Equations 12 and 14, mixed terms S_{dc} and S_{cd} of the matched circuit are no longer null.

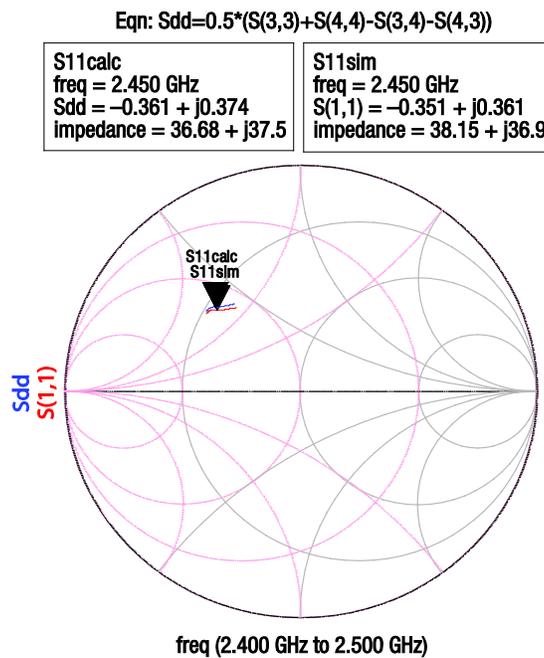


Figure 4. Comparison of Simulated vs Measured Differential Input Impedance Using the SKY65336-11 FEM

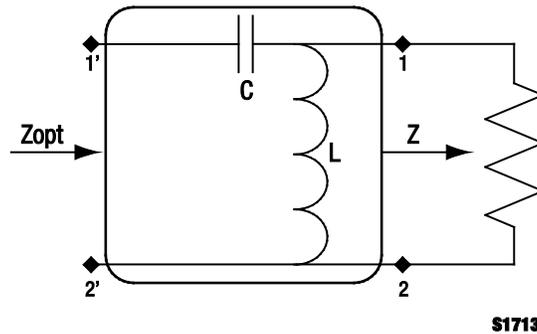


Figure 5. L-C Matching Network

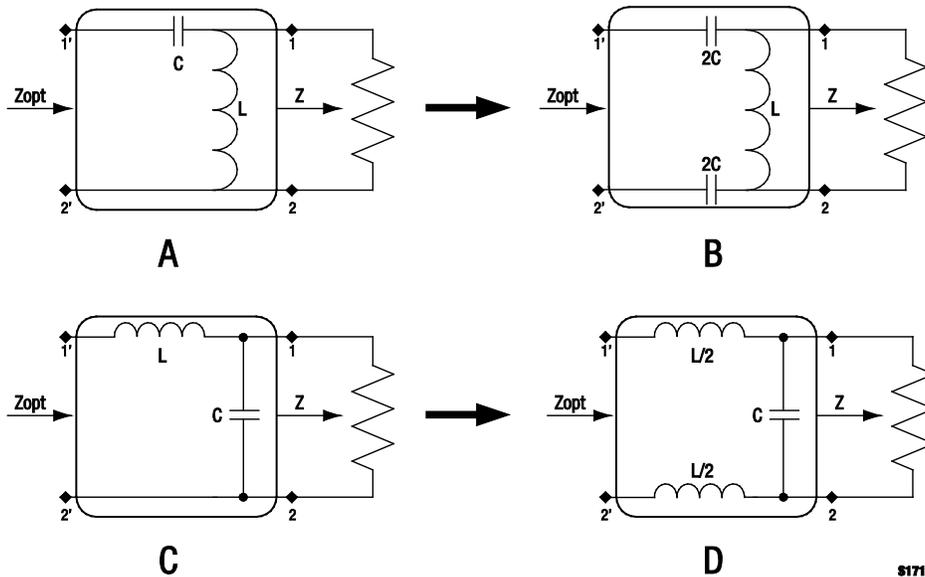


Figure 6. Single-Ended and Differential L-C Matching Equivalent Networks

The circuit symmetry can be easily realized by evaluating the impedance of the matched port, Z_{opt} , of circuit A which is given by:

$$Z_{opt} = X_C + (X_L // Z) = \frac{1}{jC\omega} + (jL\omega // Z) \quad (20)$$

Where: X_C and X_L represent the impedance (purely imaginary) of the ideal capacitor and inductor, respectively.

Equation 20 can be rewritten as:

$$Z_{opt} = \frac{1}{j2C\omega} + \frac{1}{j2C\omega} + (jL\omega // Z)$$

This equation provides the impedance of circuit B and, therefore, demonstrates that circuits A and B are equivalent. However, only circuit B maintains the symmetry ($S_{1'1'} = S_{2'2'}$).

The impedance of the circuit shown in Figure 6 (C) can be calculated by:

$$Z_{opt} = X_L + (X_C // Z) = jL\omega + (\frac{1}{jC\omega} // Z)$$

Which can be rewritten as:

$$Z_{opt} = \frac{jL\omega}{2} + \frac{jL\omega}{2} + (\frac{1}{jC\omega} // Z)$$

In this case, the circuit shown in Figure 6 (D) is equivalent to the circuit in Figure 6 (C).

Transmission Line Impedance Matching

When working with transmission line impedance matching, the simple transformation of the series element described above will not work. However, there is another simple technique available.

As shown in Figure 7 (where Z_i and L_i denote the transmission line impedance and length, respectively), the balanced differential circuit is divided into two identical half single-ended structures. The dividing line is at the ground potential because of the circuit symmetry. The result is that the series elements of both single-ended and differential circuits are identical, although the shunt element is cut in half (including the loads, Z and Z_{opt}).

Rather than matching Z to Z_{opt} , the new exercise becomes matching the half circuits, or matching $Z/2$ to $Z_{opt}/2$. Eventually, the fully differential matched circuit is derived by bringing the two half structures back together. Note that this technique can be also used with lumped elements as shown in Figure 7.

For example, a differential Z circuit and a single-ended $Z/2$ circuit are shown in Figure 8 (with $Z = 38 + j \times 37 \Omega$ and $Z/2 = 19 + j \times 18.5 \Omega$). Note that the parameter E in the transmission line model refers to the electric length or phase shift expressed in degrees:

$$E = 360 \frac{L}{\lambda}$$

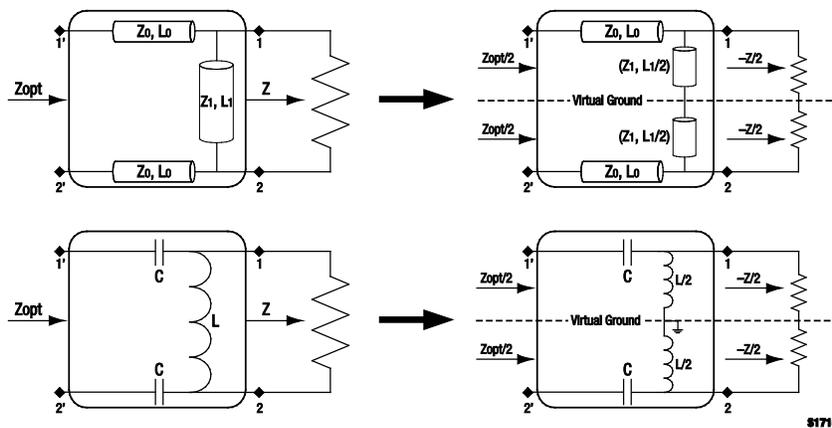


Figure 7. Differential and Half Single-Ended Matching Equivalent Networks

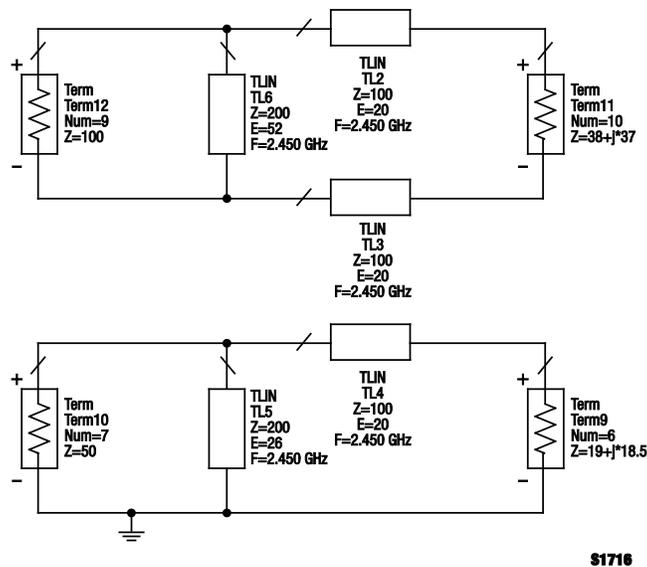


Figure 8. Example of Equivalent Differential and Half Single-Ended Matching Circuits

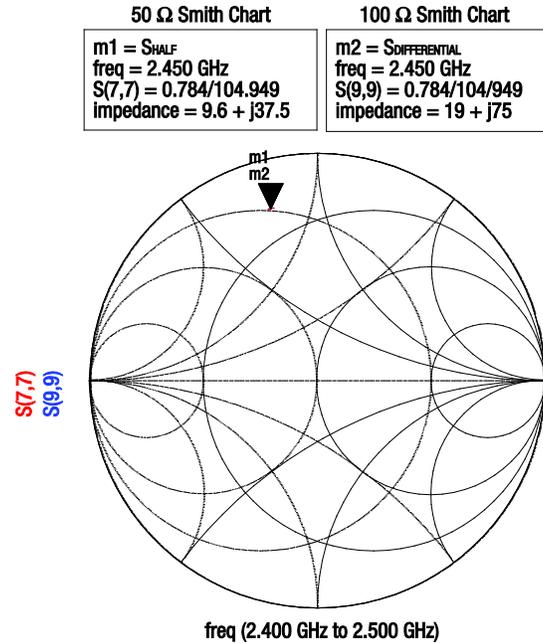


Figure 9. Impedance Comparison of Differential and Half Single-Ended Matching Circuits

Table 1. Transmit and Receive Port Differential Impedances

Device Port	SKY65336-11		SKY65337-11	
	$R_s + j(L_s \times 2 \times \pi \times f)$ (Ω)	R_p (Ω) L_p (nH)	$R_s + j(L_s \times 2 \times \pi \times f)$ (Ω)	R_p (Ω) L_p (nH)
Transmit	38 + j37	74 5	40 + j46	93 5.3
Receive	132 + j30	139 40	46.8 + j51	102 6.1

The simulation results shown in Figure 9 demonstrate that the single-ended circuit is matched to $Z_{opt}/2$ and, using the transformation described above, the differential is actually matched to Z_{opt} . Note that the Smith Chart reference impedance of the single-ended circuit is 50 Ω and 100 Ω for the differential circuit.

Matching the Differential RF Ports of the Skyworks Front-End Modules

In this section, the differential impedance matching technique is illustrated by matching the SKY65336-11 ZigBee® FEM to the Ember EM250 Transceiver.

Impedance to Match

The transmit and receive differential port S-parameters for the SKY65336-11 and SKY65337-11 FEMs have been measured and their corresponding differential impedances are listed in Table 1.

Optimum Load Impedance (Z_{opt})

Various ZigBee-compliant transceivers are available with different RF port impedances. They also specify the optimum load impedance (Z_{opt}), which represents the impedance that the transceiver should see. An optimum reflection coefficient, $0.79 \angle 65^\circ$, has been suggested [Ember, 4] (expressed in magnitude and phase) for maximum transmit power and best sensitivity. The reference impedance is 50 Ω. This corresponds to a load impedance (Z_{opt}) of $19.5 + j75$ Ω or 308 Ω || 5.2 nH.

A Matching Example Using Lumped Elements

In the following example, the SKY65336-11 transmit impedance of $Z = 38 + j37$ Ω is matched to the Ember transceiver $Z_{opt} = 19.5 + j75$ Ω. Both impedances are represented in the Smith Chart shown in Figure 10. The two traces (shown with arrows) show the course of impedance Z by adding a shunt inductor (6.8 nH) and a series inductor (2.8 nH).

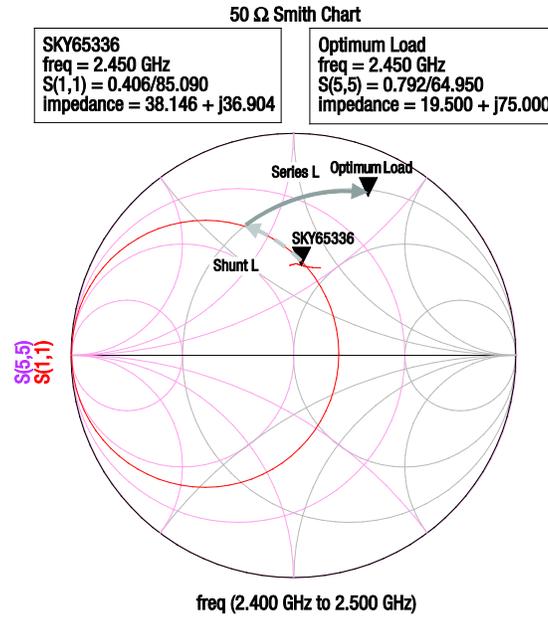


Figure 10. Shunt 6.8 nH/Series 2.8 nH Matching Example of the SKY65336-11 Transmit RF Differential Input Impedance to Ember EM250

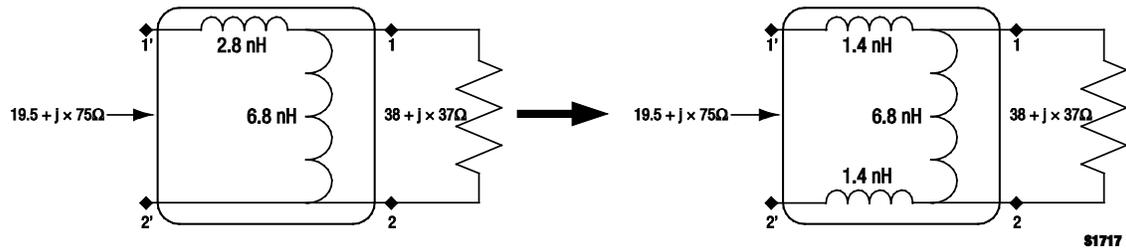


Figure 11. Circuit Transformation to Realize the Symmetry

The matching network is transformed using the technique described in the previous section and the resulting differential structure is shown in Figure 11.

To verify this exercise, the two circuits are shown in Figure 12 and the simulation results are provided in Figure 13. Together, these Figures demonstrate the compliance of the transformation.

A Matching Example Using a Combination of Lumped Elements and Transmission Lines

Even the most compact, practical board design includes transmission lines to connect the different components together [Ember, 4]. Traces from the source and load devices to the lumped matching elements contribute to impedance matching and need to be taken into account especially for high frequencies.


For a differential circuit, the two traces have to be identical to maintain the symmetry, which means the same length, width, and

distance to ground. The coupled microstrip lines structure commonly used is shown in Figure 14. The characteristic impedance of the differential mode in these transmission lines can be analyzed using the same mixed mode concept introduced earlier in this Application Note.

Assume the structure is symmetric, the differential and common modes propagate uncoupled, and the characteristic impedance of the differential mode is given by Chiariello et. al. [5]:

$$Z_{0d_microstrip} = 2Z_{o_microstrip}$$

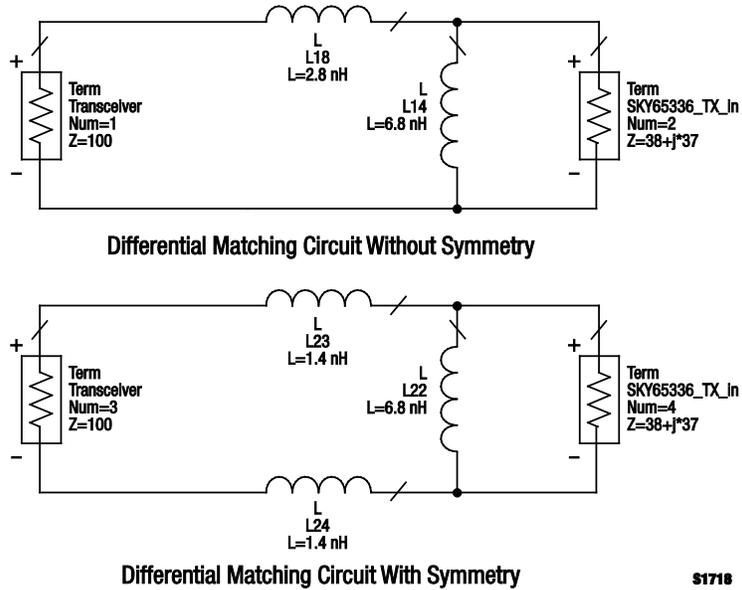Where $Z_{o_microstrip}$ is the odd mode impedance of the coupled microstrip line.



S1718

Figure 12. ADS-Lumped Element Matching Circuit Schematics


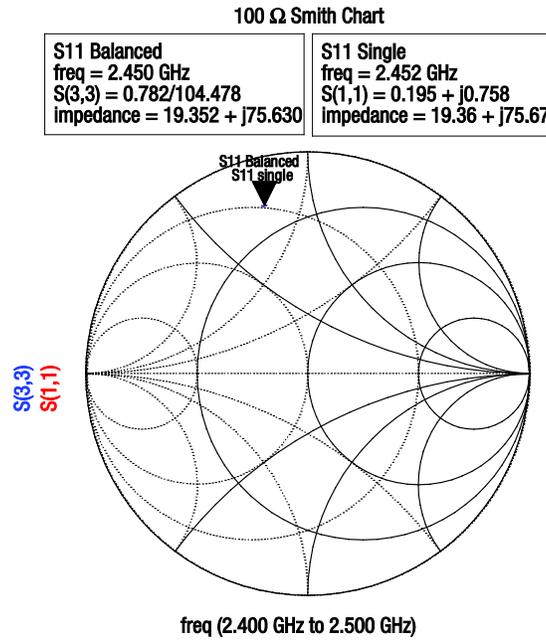


Figure 13. Comparison of the Matched Loads of the Two Circuits Shown in Figure 12

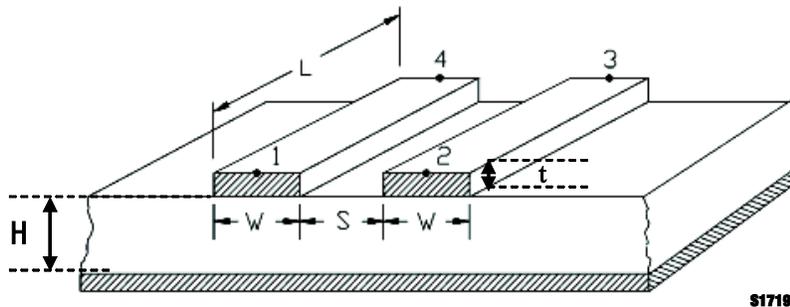

S1719

Figure 14. Coupled Microstrip Lines Structure

As a first order approximation, assume the ideal case where the distance between the two single-ended lines, S , is one order of magnitude larger than their width, W . As a result, unwanted coupling between them is negligible. In this case, the differential impedance is simply given by Bockelman et. al. [1]:

$$Z_{0d_microstrip} = 2Z_{0_microstrip}$$

Where $Z_{0_microstrip}$ is the characteristic impedance of the single microstrip line.


The transmission impedance needed to connect the different devices still needs to be determined. Usually, 50Ω trace impedance is used as a standard to interconnect single-ended devices. For differential devices, several standard impedances (e.g., $50, 75, 100 \Omega$) are widely used. PCB stack-up constraints include minimum reliable trace width and PCB cost; both contribute to the final design.

Assume the following PCB stack-up:

- $H = 8$ mil
- $Er = 4.3$
- Cond = $59.6e+6$ Siemens/meter
- $t = 1.4$ mil
- TanD = 0.02

A 75Ω reference impedance transmission line design has narrower traces compared to a 50Ω line. That allows such a design to be spaced out more to minimize the coupling, which is always difficult to estimate. The matching circuit shown in Figure 15 is composed of two identical 75Ω transmission lines, TL1 and TL2, and one shunt inductor, L1, that tune the load impedance $Z/2$ to $Z_{opt}/2$.

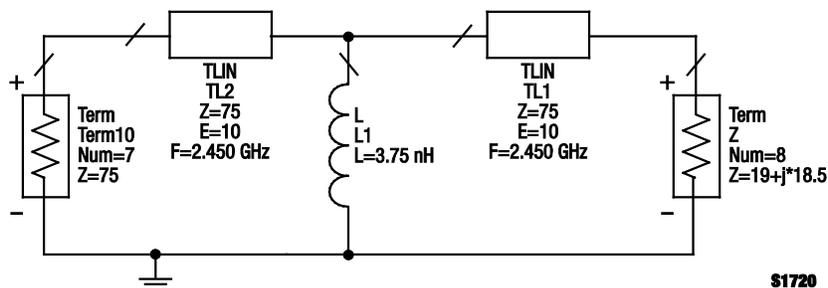Since a 75Ω trace impedance is used for matching in this example, the Smith Chart reference impedance should also be 75Ω so that when a transmission line is added to the load, Z , the impedance navigates on a constant VSWR circle shown in Figure 16.



S1720

Figure 15. Ideal Single-Ended Matching Circuit Schematic Using Distributed and Lumped Elements

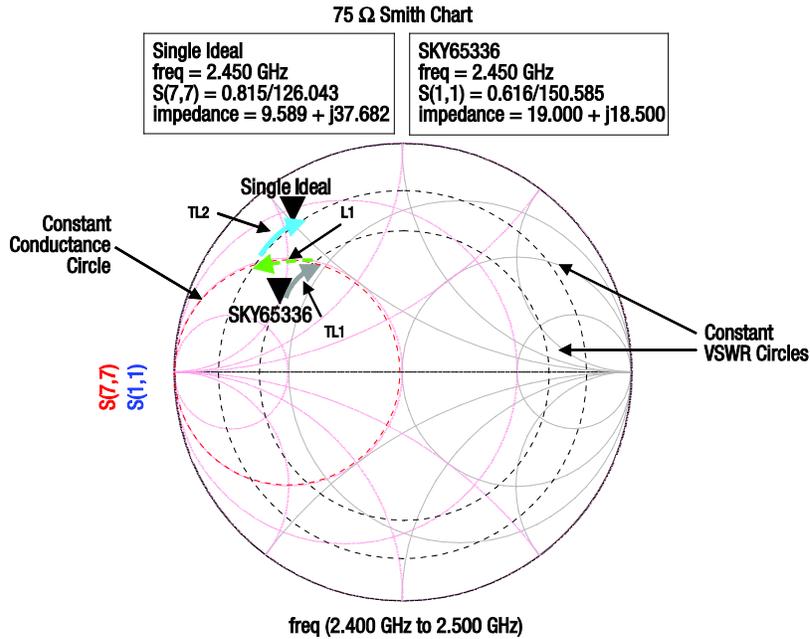


Figure 16. Impedance of Single-Ended Ideal Matching Circuit Using a Combination of Distributed and Lumped Elements

To create a microstrip line with an impedance of 75 Ω and an electrical length of 10°, Equations 21 and 22 are used to compute the width ($W = 6$ mils) and the length of the microstrip line ($L = 80$ mils).

$$W = \frac{(5.98 \times H e^{-(Z_0 \cdot \frac{(\sqrt{\epsilon_r + 1.41})}{87}) - t})}{0.8} \quad (21)$$

Where H is the dielectric thickness (8 mils), ϵ_r is the dielectric relative permittivity, and t is the conductor thickness.

$$L = \frac{E}{T \times f_0 \times 360} \quad (22)$$

Where f_0 is the frequency (2.45 GHz), E is the electrical length (10°), and T is the propagation delay:

$$T = 85 \times e^{-15} \sqrt{(0.475 \times \epsilon_r + 0.67)} (s / mil)$$

The actual single-ended structure is shown in Figure 17.

Assuming there is no coupling between the two single-ended transmission lines, the differential structure as described in the previous section is derived by combining the two single-ended structures as shown in Figure 18.

Eventually, the results are compared on a Smith Chart (see Figure 19) and it can be confirmed that the differential matched load – S(5,5) on the plot – is $Z_{opt} (19.5 + j75 \Omega)$. Note that this


point on the chart is slightly different because of the approximation of the transmission line (negligible coupling between the two microstrip lines). However, because the matched load is very close, the approximation has no effect on performance.

Conclusions

Common opinion is that matching differential port devices is a difficult task compared to matching single-ended devices, and can only be achieved using advanced and expensive tools such as four-port differential network analyzers. This Application Note demonstrates that matching differential port devices does not require any additional tools and that once the different tasks have been clearly identified, it becomes a fairly simple exercise.


Determining the differential load can be achieved using two-port network analyzer measurements together with a simple calculation as expressed in Equation 19.

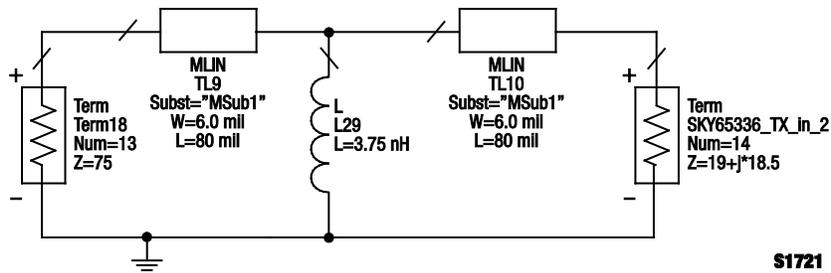Matching techniques can also be performed using a Smith Chart and applying simple circuit transformations as depicted in Figures 6 and 7.



S1721

Figure 17. Actual Single-Ended Matching Circuit Schematic Using Distributed and Lumped Elements

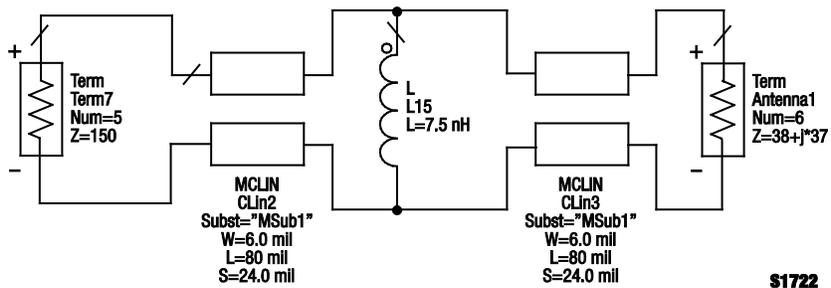

S1722

Figure 18. Actual Differential Matching Circuit Schematic Using Distributed and Lumped Elements

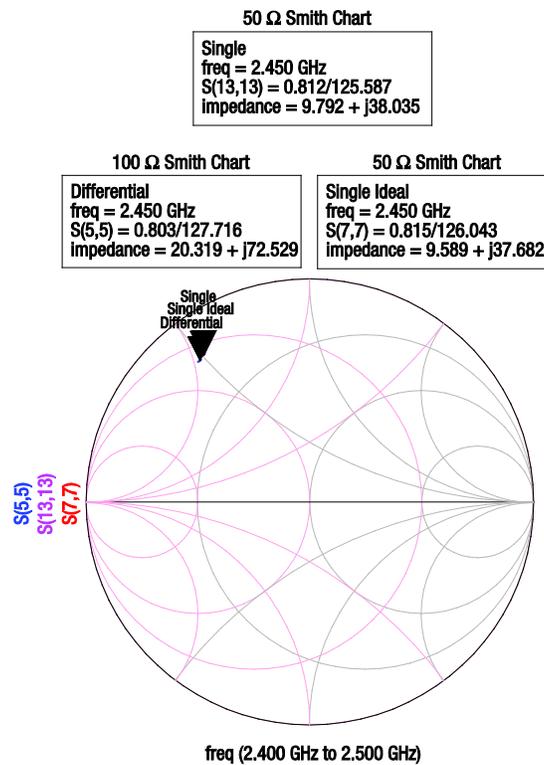


Figure 19. Impedance of Single-Ended Ideal/Actual and Differential Matching Circuits Using a Combination of Distributed and Lumped Elements

References

1. Bockelman, David E. and William R. Eisenstadt. *Combined Differential and Common-Mode Scattering Parameters: Theory and Simulation*, IEEE Transactions on Microwave Theory and Techniques, Vol. 43, No. 7, July 1995.
2. Bockelman, David E. and William R. Eisenstadt. *Pure-Mode Network Analyzer for On-Wafer Measurements of Mixed-Mode S-Parameters of Differential Circuits*, IEEE Transactions on Microwave Theory and Techniques, Vol. 45, No. 7, July 1997.
3. *PCB Design With an EM250*. Ember Application Note 5059, 27 March 2009.
4. Front-End Module reference design files located at http://ember.com/zip/REF_DES_SKY65336_SKY65337.zip.
5. Chiariello, A.G., A. Maffucci, G. Miano, F. Villone, and W. Zamboni. *A Transmission-Line Model for Full-Wave Analysis of Mixed-Mode Propagation*, IEEE Transactions on Advanced Packaging, Vol. 31, No. 2, May 2008.

Copyright © 2009, 2012 Skyworks Solutions, Inc. All Rights Reserved.

Information in this document is provided in connection with Skyworks Solutions, Inc. ("Skyworks") products or services. These materials, including the information contained herein, are provided by Skyworks as a service to its customers and may be used for informational purposes only by the customer. Skyworks assumes no responsibility for errors or omissions in these materials or the information contained herein. Skyworks may change its documentation, products, services, specifications or product descriptions at any time, without notice. Skyworks makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Skyworks assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Skyworks products, information or materials, except as may be provided in Skyworks Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. SKYWORKS DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. SKYWORKS SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Skyworks products are not intended for use in medical, lifesaving or life-sustaining applications, or other equipment in which the failure of the Skyworks products could lead to personal injury, death, physical or environmental damage. Skyworks customers using or selling Skyworks products for use in such applications do so at their own risk and agree to fully indemnify Skyworks for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Skyworks products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Skyworks assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Skyworks products outside of stated published specifications or parameters.

Skyworks, the Skyworks symbol, and "Breakthrough Simplicity" are trademarks or registered trademarks of Skyworks Solutions, Inc., in the United States and other countries. Third-party brands and names are for identification purposes only, and are the property of their respective owners. Additional information, including relevant terms and conditions, posted at www.skyworksinc.com, are incorporated by reference.